
# 9.5.4. Design example

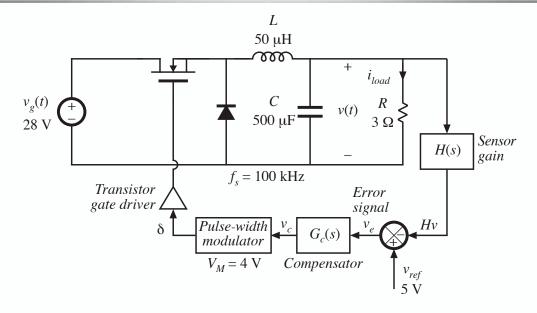

Fundamentals of Power Electronics

46

Chapter 9: Controller design

# Quiescent operating point

Input voltage	$V_g = 28V$
---------------	-------------

Output 
$$V = 15V$$
,  $I_{load} = 5A$ ,  $R = 3\Omega$ 


Quiescent duty cycle 
$$D = 15/28 = 0.536$$

Reference voltage 
$$V_{ref} = 5V$$

Quiescent value of control voltage 
$$V_c = DV_M = 2.14V$$

Gain 
$$H(s)$$
  $H = V_{ref}/V = 5/15 = 1/3$ 

### Small-signal model

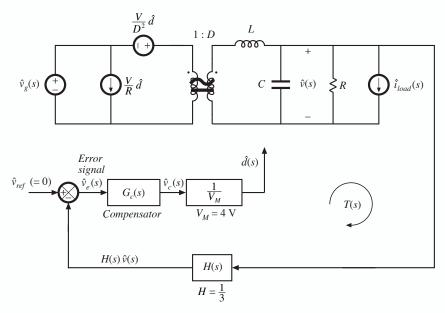


Fundamentals of Power Electronics

48

Chapter 9: Controller design
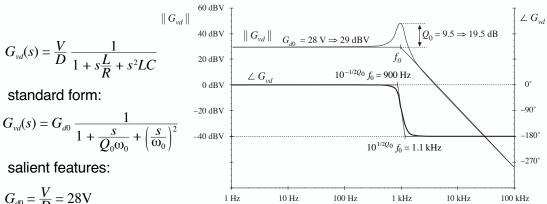
## Open-loop control-to-output transfer function $G_{vd}(s)$



$$G_{d0} = \frac{V}{D} = 28V$$

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}} = 1\text{kHz}$$

$$Q_0 = R\sqrt{\frac{C}{L}} = 9.5 \Rightarrow 19.5\text{dB}$$

# Open-loop line-to-output transfer function and output impedance

$$G_{vg}(s) = D \frac{1}{1 + s\frac{L}{R} + s^2 LC}$$

—same poles as control-to-output transfer function standard form:

$$G_{vg}(s) = G_{g0} \frac{1}{1 + \frac{s}{Q_0 \omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

Output impedance:


$$Z_{out}(s) = R \parallel \frac{1}{sC} \parallel sL = \frac{sL}{1 + s\frac{L}{R} + s^2LC}$$

Fundamentals of Power Electronics


50

Chapter 9: Controller design

#### System block diagram

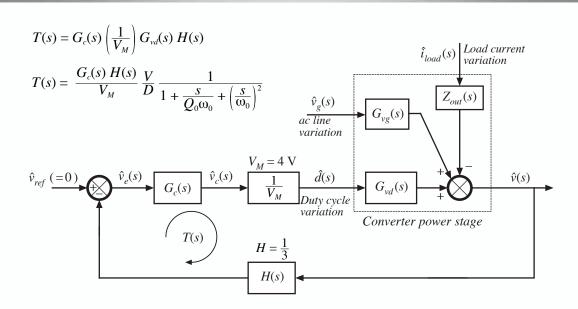
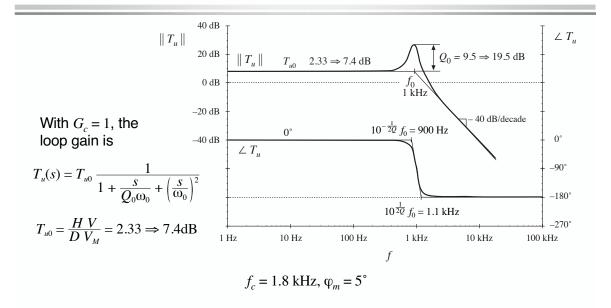
## Uncompensated loop gain (with $G_c = 1$ )



Fundamentals of Power Electronics

52

Chapter 9: Controller design


#### Lead compensator design

- Obtain a crossover frequency of 5 kHz, with phase margin of 52°
- $T_u$  has phase of approximately  $180^{\circ}$  at 5 kHz, hence lead (PD) compensator is needed to increase phase margin.
- Lead compensator should have phase of + 52° at 5 kHz
- $T_u$  has magnitude of 20.6 dB at 5 kHz
- Lead compensator gain should have magnitude of + 20.6 dB at 5 kHz
- · Lead compensator pole and zero frequencies should be


$$f_z = (5\text{kHz}) \sqrt{\frac{1 - \sin(52^\circ)}{1 + \sin(52^\circ)}} = 1.7\text{kHz}$$
  
 $f_p = (5\text{kHz}) \sqrt{\frac{1 + \sin(52^\circ)}{1 - \sin(52^\circ)}} = 14.5\text{kHz}$ 

• Compensator dc gain should be  $G_{c0} = \left(\frac{f_c}{f_0}\right)^2 \frac{1}{T_{u0}} \sqrt{\frac{f_z}{f_p}} = 3.7 \Rightarrow 11.3 \mathrm{dB}$ 


# Lead compensator Bode plot

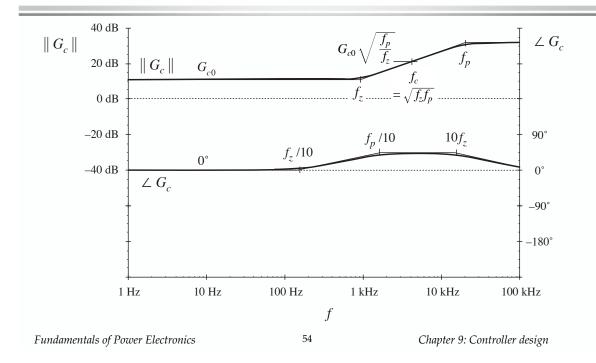


# Loop gain, with lead compensator

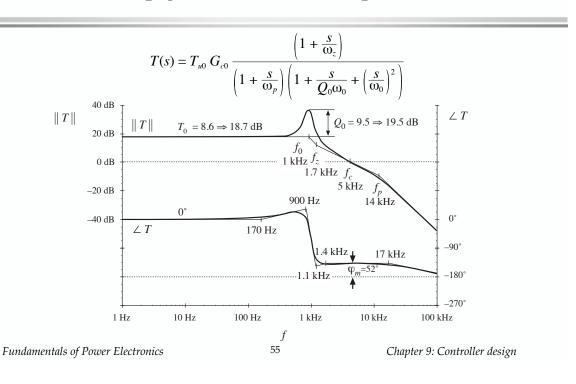


# 1/(1+T), with lead compensator

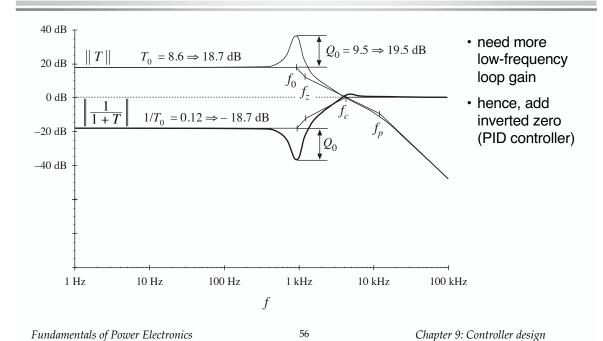


### Improved compensator (PID)

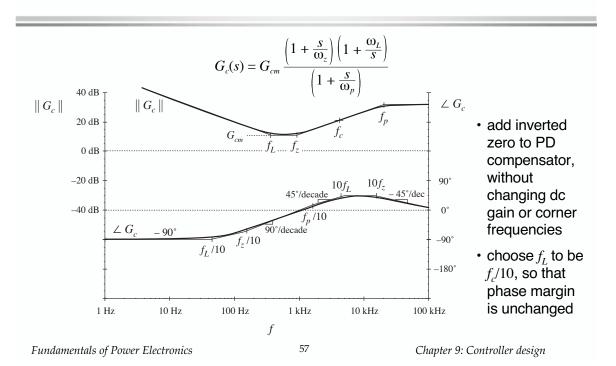
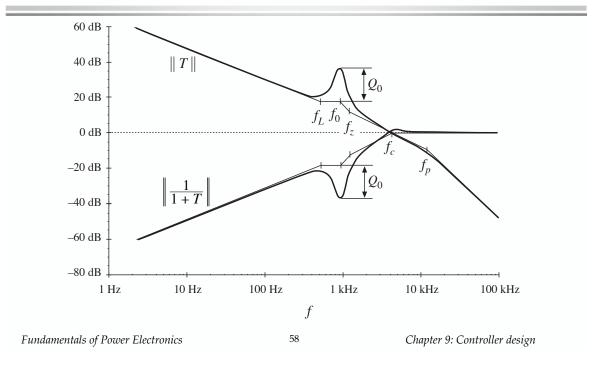
# T(s) and 1/(1+T(s)), with PID compensator




# Line-to-output transfer function

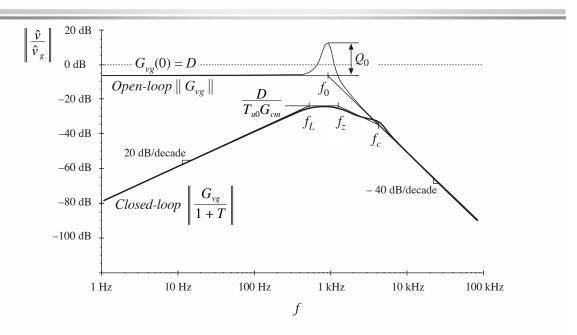
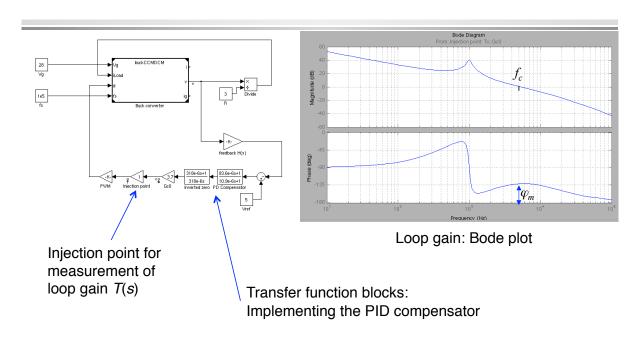
# Closed-loop buck converter

Simulink frequency domain simulation, averaged model



## Closed-loop line-to-output transfer function Simulink frequency domain simulation

